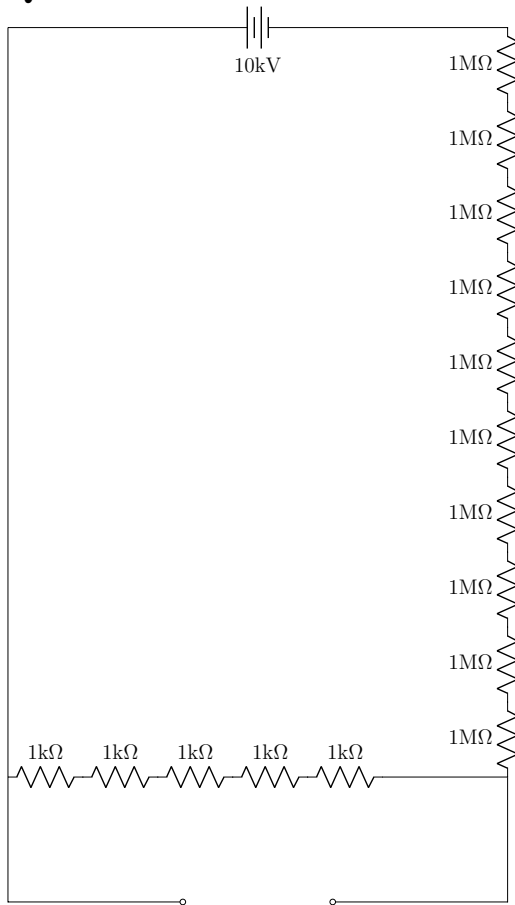


# HW Set 1

Johannes Byle

October 26, 2020

## Question 1



Assuming the data monitoring system can be modeled as a short, the total current across the circuit is  $I = \frac{10 \text{ kV}}{10 \text{ M}\Omega + 5 \text{ k}\Omega} \approx 10^{-5} \text{ A}$ . Thus the maximum power dissipated by any single resistor cannot be more than  $P = I^2 R =$

$$(10^{-5})^2 \text{ A} \times 1 \text{ M}\Omega \approx 1 \text{ W}$$

### Question 2

$$-16 = -2I_1 - 2(I_1 + I_2) - I_1 + I_3$$

$$-9 = -2(I_2 + I_3) - 2(I_2 + I_1) - I_2$$

$$0 = -4I_3 - I_3 + I_1 - 2(I_3 + I_2)$$

$$\begin{bmatrix} -5 & -2 & 1 \\ -2 & -5 & -2 \\ 1 & -2 & -7 \end{bmatrix}^{-1} \begin{bmatrix} -16 \\ -9 \\ 0 \end{bmatrix} \approx \begin{bmatrix} 3.1 \\ 0.4 \\ 0.3 \end{bmatrix}$$

### Question 3

$$-16 = -r_1 I_1 - r_3(I_1 + I_2) - L_4\left(\frac{\delta I_1}{\delta t} + \frac{\delta I_3}{\delta t}\right)$$

$$-9 = -r_5(I_2 + I_3) - r_3(I_2 + I_1) - L_2 \frac{\delta I_2}{\delta t}$$

$$0 = -r_6 I_3 - r_4(I_3 - I_1) - r_5(I_3 + I_2)$$