
HW Set 3

Johannes Byle

November 11, 2020

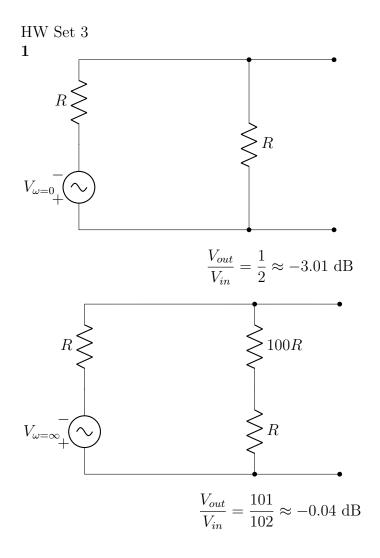


2 Its a low pass filter.


$$H = \frac{\frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}}$$

$$|H| = \frac{1}{\left(CL\omega^2 - 1\right)^2}$$

$$\omega = \sqrt{1 + \sqrt{2}}\sqrt{\frac{1}{CL}} = \sqrt{\frac{1 - \sqrt{2}}{1 \cdot 1 \cdot 10^{-6}}} \approx 1554$$

$$f = 247 \text{ Hz}$$

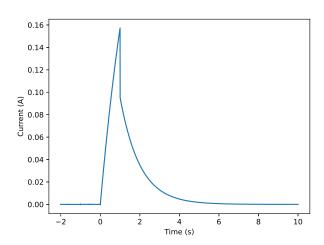

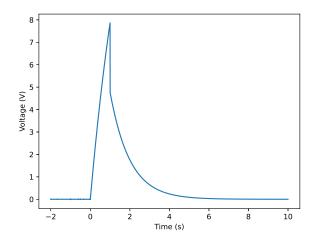

```
import numpy as np
import matplotlib.pyplot as plt
from scipy.integrate import quad
t = np. linspace(-2, 10, 10000)
v = np.zeros(np.shape(t))
v[(t < 1) & (0 < t)] = 40
r = np. zeros(np. shape(t))
r[(t \le 1) \& (0 < t)] = 100
r[t > 1] = 200
L = 200
def integral (time):
    \mathbf{def} \ \mathbf{f}(\mathbf{x}):
         if x < 0:
             V = 0
             R = 0
         elif 0 \le x < 1:
             V = 40
             R = 100
         else:
             V = 0
             R = 200
        return (np.exp((R * x) / L) * V) / L
    y, err = quad(f, 1, time)
    return y
f = np.array([integral(n) for n in t])
i = np.exp(-(r * t) / L) * (f - f[0])
plt.plot(t, i)
plt.plot(t, i * 50)
plt.show()
```

This code simply plots the following equation for the given parameters.

$$e^{-\frac{Rt}{L}}\left(\int_{1}^{t}\frac{e^{\frac{R\xi}{L}}V\left(\xi\right)}{L}d\xi+C\right)$$

The code could have been a lot shorter and simpler, but I had to write my own function for the integral portion of the equation.

4.a


$$\omega_r = \frac{1}{\sqrt{LC}}$$

$$C = \frac{1}{L\omega_r^2} = \frac{1}{0.1\cdot 100^2} = 0.001 \text{ F}$$

At this condition the imaginary component is zero, and its called the resonance frequency.

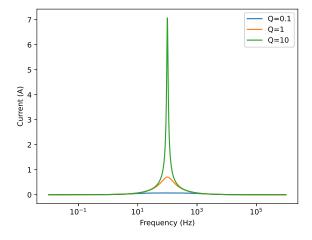4.b

$$Q = \frac{\omega_0 L}{R}$$
$$R = \frac{\omega_0 L}{Q}$$



import numpy as np

```
C = 0.001
L = 0.1
R_{-1} = (100 * L) / 0.1
R_{-2} = (100 * L) / 1
R_{-3} = (100 * L) / 10
\mathbf{def} \ \mathbf{z}(\mathbf{w}, \ \mathbf{R}):
     val = R + 1 / (1j * w * C) + 1j * w * L
     return (10 / np.sqrt(np.real(val * np.conj(val)))) / (np.sqrt(2))
w = np. linspace (10 ** (-2), 10 ** 6, 1000000)
plt.\,plot\,(w,\ z\,(w,\ R_{-}1\,)\,,\ label="Q=0.1"\,)
plt.plot(w, z(w, R<sub>-</sub>2), label="Q=1")
plt.plot(w, z(w, R<sub>-</sub>3), label="Q=10")
plt.xlabel("Frequency_(Hz)")
plt.ylabel("Current_(A)")
plt.xscale("log")
# plt.yscale("log")
plt.legend()
plt.show()
```

import matplotlib.pyplot as plt