

HW Set 2


Johannes Byle

November 2, 2020

1.a $Z = R + j\omega L$

1.b $f = \text{linspace}(0, 10, 1001);$

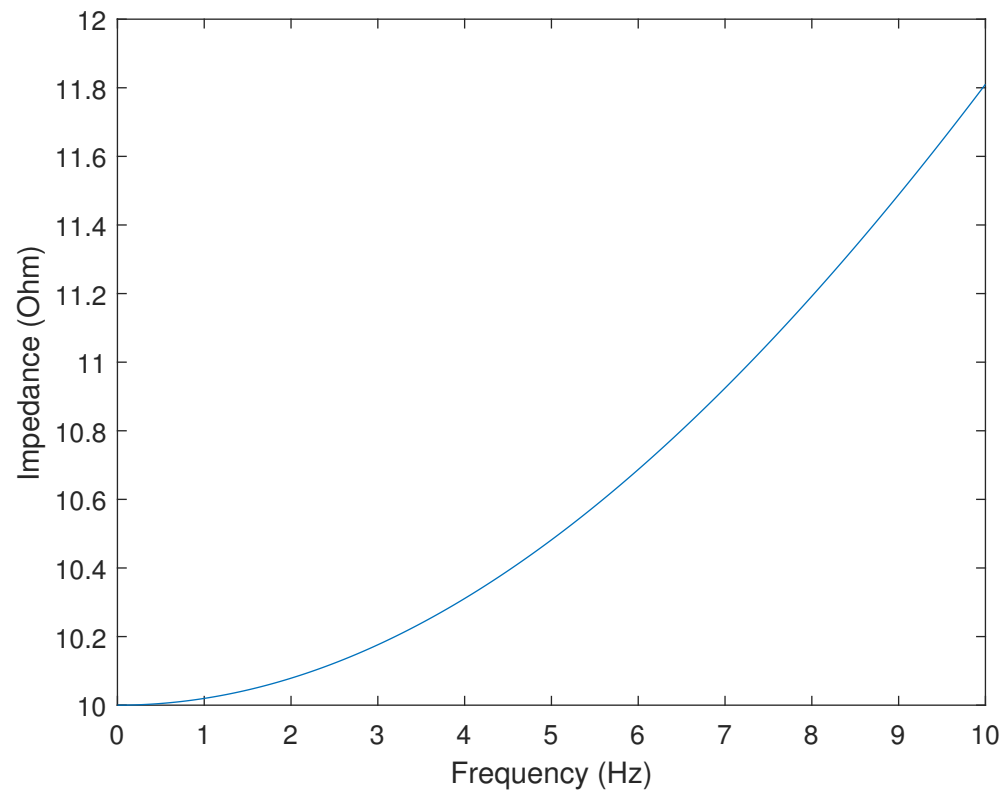1.c $Z = 10 + 1i \cdot 2 \cdot \pi \cdot 10 \cdot 10^3 \cdot f;$



1.d

1.e At the low frequency the R^2 term dominates, and thus the line starts of

horizontal, however at high frequencies the $\omega^2 L^2$ term dominates, and since the whole thing is under a square root it approaches a straight line function.

2.a $Z = \left(\frac{1}{Z_R} + \frac{1}{Z_C} + \frac{1}{Z_L} \right)$

$Z_R = R, \quad Z_C = \frac{1}{j\omega C}, \quad Z_L = j\omega L$

$Z_{tot} = \left(\frac{1}{R} + j\omega C + \frac{1}{j\omega L} \right)$

2.b $|Z| = \sqrt{\left(\frac{1}{R} + j\omega C + \frac{1}{j\omega L} \right) \left(\frac{1}{R} - j\omega C - \frac{1}{j\omega L} \right)} = \sqrt{\frac{1}{R^2} + \frac{(\omega^2 CL - 1)^2}{\omega^2 L^2}}$

2.c $V_0 e^{j\frac{\pi}{2}}$ The magnitude is V_0 and the phase is $\frac{\pi}{2}$.

2.d $\tilde{I}_s = \frac{\tilde{V}_s}{\tilde{Z}_s} = \frac{V_0 e^{j\frac{\pi}{2}}}{\left(\frac{1}{R} + j\omega C + \frac{1}{j\omega L} \right)}$


$|\tilde{I}_s| = \left(\frac{V_0 e^{j\frac{\pi}{2}}}{\left(\frac{1}{R} + j\omega C + \frac{1}{j\omega L} \right)} \right) \left(\frac{V_0 e^{-j\frac{\pi}{2}}}{\left(\frac{1}{R} - j\omega C - \frac{1}{j\omega L} \right)} \right) = \frac{LRV_0\omega}{\sqrt{R^2(CL\omega^2 - 1)^2 + L^2\omega^2}}$

2.e $\tilde{I}_R = \frac{V_0 e^{j\frac{\pi}{2}}}{R}$


$\tilde{I}_C = V_0 e^{j\frac{\pi}{2}} j\omega C$

$\tilde{I}_L = \frac{V_0 e^{j\frac{\pi}{2}}}{j\omega L}$

3.a If the frequency is very low:

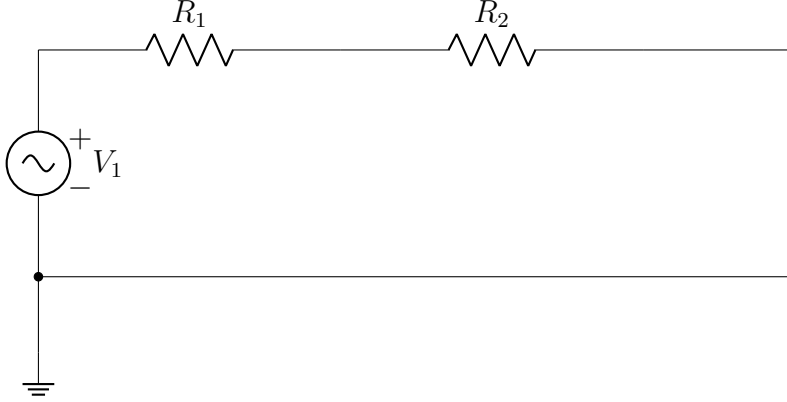

If the frequency is very high:

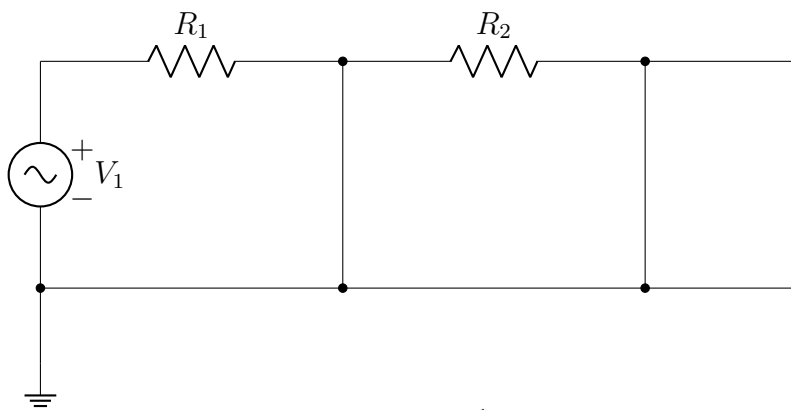

3.b $Z = R_1 + \left(j\omega C_1 + \frac{1}{R_2 + \frac{1}{j\omega C_2}} \right)^{-1}$

3.c $\tilde{I}_{tot} = \frac{\tilde{V}_1 e^{j\phi}}{R_1 + \left(j\omega C_1 + \frac{1}{R_2 + \frac{1}{j\omega C_2}} \right)^{-1}}$